



higher education & training

Department:
Higher Education and Training
REPUBLIC OF SOUTH AFRICA

T60(E)(A6)T

NATIONAL CERTIFICATE

ARMATURE WINDING THEORY N2

(11020042)

6 April 2018 (X-Paper)

09:00–12:00

Calculators may be used.

This question paper consists of 4 pages and a formula sheet of 3 pages.

DEPARTMENT OF HIGHER EDUCATION AND TRAINING
REPUBLIC OF SOUTH AFRICA
NATIONAL CERTIFICATE
ARMATURE WINDING THEORY N2
TIME: 3 HOURS
MARKS: 100

INSTRUCTIONS AND INFORMATION

1. Answer ALL the questions.
 2. Read ALL the questions carefully.
 3. Number the answers according to the numbering system used in this question paper.
 4. Diagrams must be neat and in proportion.
 5. Use $\pi = 3,142$.
 6. Work neatly.
-

QUESTION 1

- 1.1 A six-pole wave-wound armature has 80 slots, 320 commutator segments and single-turn coils.
- 1.1.1 Make a neat, labelled sketch of the coil sides as they are arranged in each slot. (10)
- 1.1.2 Find a suitable coil span. (3)
- 1.1.3 Find a suitable commutator pitch. (3)
- 1.2 What is *armature reaction*? (3)
- [19]**

QUESTION 2

Draw neat, labelled diagrams to show each of the following:

- 2.1 Reversal of direction of rotation of a shunt motor (6)
- 2.2 Reversal of direction of rotation of a series motor (6)
- 2.3 Reversal of direction of a long-shunt motor (8)
- [20]**

QUESTION 3

A series circuit consists of a resistor of 5 ohms, an inductor of 0,01 henry and a capacitor of 75 microfarad connected to a 200 V/100 Hz supply.

Calculate the following:

- 3.1 Total current (8)
- 3.2 Phase angle (2)
- 3.3 Potential difference across each component (6)
- [16]**

QUESTION 4

- 4.1 What is the purpose of a centrifugal switch in a single-phase motor? (3)
- 4.2 Make a neat, labelled sketch of a single-phase transformer. (4)
- 4.3 How efficient is a transformer? (1)
- 4.4 A three-phase delta/star transformer supplies a line current of 900 amperes to a load.
- Calculate the following if the primary line voltage is 6,6 kV and the secondary line voltage is 380 V:
- 4.4.1 Primary and secondary phase voltages (3)
- 4.4.2 Transformation ratio (3)
- 4.4.3 Primary line current (6)
- [20]**

QUESTION 5

- 5.1 Make neat, labelled sketches to show the reversal of rotation of a three-phase induction motor. (6)
- 5.2 Explain how the rotating magnetic field operates in a three-phase induction motor. (4)
- [10]**

QUESTION 6

Draw a neat data sheet giving all the information required before an armature is rewinded. **[11]**

QUESTION 7

Draw and label a section of armature slots with coils. **[4]**

TOTAL: 100

ARMATURE WINDING THEORY N2

FORMULA SHEET

$$1. \quad \text{COIL SPAN} = \frac{\text{Total number of slots} + 1}{\text{Total number of poles}}$$

$$\text{SPOELSPAN} = \frac{\text{Totale aantal gleuwe} + 1}{\text{Totale aantal pole}} =$$

$$2. \quad \text{COMMUTATOR PITCH} = \frac{\text{Number of segments} \pm 1}{\text{Number of pairs of poles}}$$

$$\text{KOMMUTATORSTEEK} = \frac{\text{Hoeveelheid segmente} \pm 1}{\text{Hoeveelheid poolpare}}$$

$$3. \quad E = \frac{\text{Total flux of pole}}{\text{Time of one revolution}}$$

$$= 2p \phi \div \frac{60}{N}$$

$$= \frac{2 \phi NP}{60} \text{ volt}$$

$$E = \frac{\text{Totale vloed van pole}}{\text{Duur van een omwenteling}}$$

$$E = \frac{2 ZNP \phi}{C \times 60}$$

$$Z = \frac{EXC \times 60}{2 NP \phi}$$

$$\text{MECHANICAL POWER} = \frac{\text{Force} \times \text{distance}}{\text{Time in seconds}}$$

$$= 2 \pi \text{ metres}$$

$$\therefore P = F \times 2 \pi R \times \frac{N}{60}$$

$$= \frac{2 \pi NT}{60} \text{ watts}$$

$$\text{MEGANIESE DRYWING} = \frac{\text{Krag} \times \text{afstand}}{\text{Tyd in sekondes}}$$

$$E = V + I_a R_a \text{ or/of } E = V - I_a R_a$$

$$V = E + I_a R_a$$

SUMMARY

$$E = \frac{2 ZNP\phi}{C \times 60}$$

$$T = \frac{ZP\phi I_a}{C \times \pi}$$

$$A = \frac{I}{J}$$

$$E = V + I_a R_a \quad A_{\max/\text{maks}} = \frac{I_a}{J_{\min}}$$

$$I_a = I + I_f \quad A_{\min} = \frac{I_a}{J_{\max/\text{maks}}}$$

$$P = EI_a$$

$$L_t = Z \times \frac{\text{Length per turn}}{2}$$

$$L_t = Z \times \frac{\text{Lengte per draai}}{2}$$

$$R_a = Z \times \frac{\text{Length per turn} \times \text{Resistance per unit}}{C^2}$$

$$R_a = Z \times \frac{\text{Lengte per draai} \times \text{Weerstand per eenheid}}{C^2}$$

*RECTANGULAR CONDUCTORS**REGHOEKIGE GELEIERS*

$$R = \frac{\rho \ell}{A}$$

$$R_a = \frac{I_t \times \text{resistance per unit length}}{C^2}$$

$$R_a = \frac{I_t \times \text{weerstand per eenheid lengte}}{C^2}$$

$$A_{\max} = \frac{I_a}{J_{\min}}$$

$$A_{\text{maks}} = \frac{I_a}{J_{\min}}$$

$$A_{\min} = \frac{I_a}{J_{\max}}$$

$$A_{\min} = \frac{I_a}{J_{\text{maks}}}$$

$$n = f/p$$

$$QV^2 = QR^2 + QL^2$$

$$\frac{VP}{VS} = \frac{NP}{NS} = \frac{IS}{IP}$$

$$V^2 = (IR)^2 + (I \times L)^2$$

$$V = I \sqrt{R^2 + XL^2}$$

$$\frac{V}{I} = \sqrt{R^2 + XL^2}$$

$$Z = \sqrt{R^2 + XC^2}$$

$$XL = 2 \pi FL$$

$$Z = \sqrt{R^2 + XL^2}$$

$$C = \frac{Q}{V}$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{V}{I} = \frac{1}{2\pi} FC$$

$$I = \frac{V}{Z}$$

$$C = \frac{I}{2\pi} FX_C$$

$$Z = \sqrt{R^2 + (X_C - XL)^2}$$

$$\cos \phi = \frac{R}{Z}$$

$$I_p N_p = I_s N_s$$

$$\frac{I_p}{I_s} = \frac{N_s}{N_p}$$

$$\frac{I_P}{I_S} = \frac{N_s}{N_p} = \frac{V_s}{V_p}$$

$$\text{Current} = \frac{\text{Apparent power} \cdot Ps}{\text{Potential difference} \cdot V}$$

$$\text{Stroom} = \frac{\text{Skyndrywing} \cdot Ps}{\text{Potensiaalverskil} \cdot V}$$